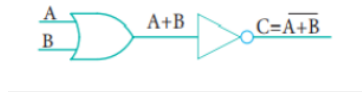


# 1 NOR Gate

The NOR (NOT OR) gate circuit is an inverter OR gate Reads as  $C = \text{NOT of A or B}$

The NOR Gate gives a true output (result of 1) only when both inputs are false (0)



## 1.1 NB

The NOR Gate is a universal gate because it can be used to form any other kind of gate

Symbol		Truth Table		
A	B	Q		
0	0	1		
0	1	0		
1	0	0		
1	1	0		

Boolean Expression  $Q = A \text{ NOR } B$