

# 1 Logic Gates

Logic Gates perform logical operations that take binary inputs (0s and 1s) and produce a single binary output. They are used in most electronic devices including:

Table 1: Logic Gates

Smartphones	Tablets	Memory Devices
		