

# 1 Logic Gates

Logic gates perform logical operations that take binary input (0s and 1s) and produce a single binary output. They are used in most electronic device including

