

1 NOT Gate

The NOT gate is called a logical inverter. It has only one input. It reverses the original input (A) to give an inverted output C. $C = \text{NOT } A$

