1 XNOR Gate

The XNOR (exclusive - NOR) gate is a combination XOR gate followed by an inverter. It is represented by the dot and the circle surrounding it. Its gives a true output (1), if the inputs are the same, and a false output (0) if the inputs are different.